



MEC4126F: Integrated Embedded Systems

Prac 7
08 May 2025

Total marks: 51

Instructions to students

1. This template file contains space for the answers to the written questions of Prac 7.
2. Ensure that you copy-paste your answers inside the space allocated for each question.
3. Provide your numerical answers to **TWO (2)** significant decimal points, unless stated otherwise.

PeopleSoft ID: MTNJW 002

Plagiarism Declaration

By demonstrating and submitting this practical I agree that:



- I know that plagiarism is a serious form of academic dishonesty.
- I have read the document about avoiding plagiarism, am familiar with its contents and have avoided all forms of plagiarism mentioned there.
- Where I have used the words of others, I have indicated this by the use of quotation marks.
- I have referenced all quotations and other ideas borrowed from others.
- I have not and shall not allow others to plagiarise my work.
- I have not used an AI language model to generate the code or answers submitted here.

Name: Justice Motaung

Signature: 

Question 1 (6 marks)

Circuit Diagram

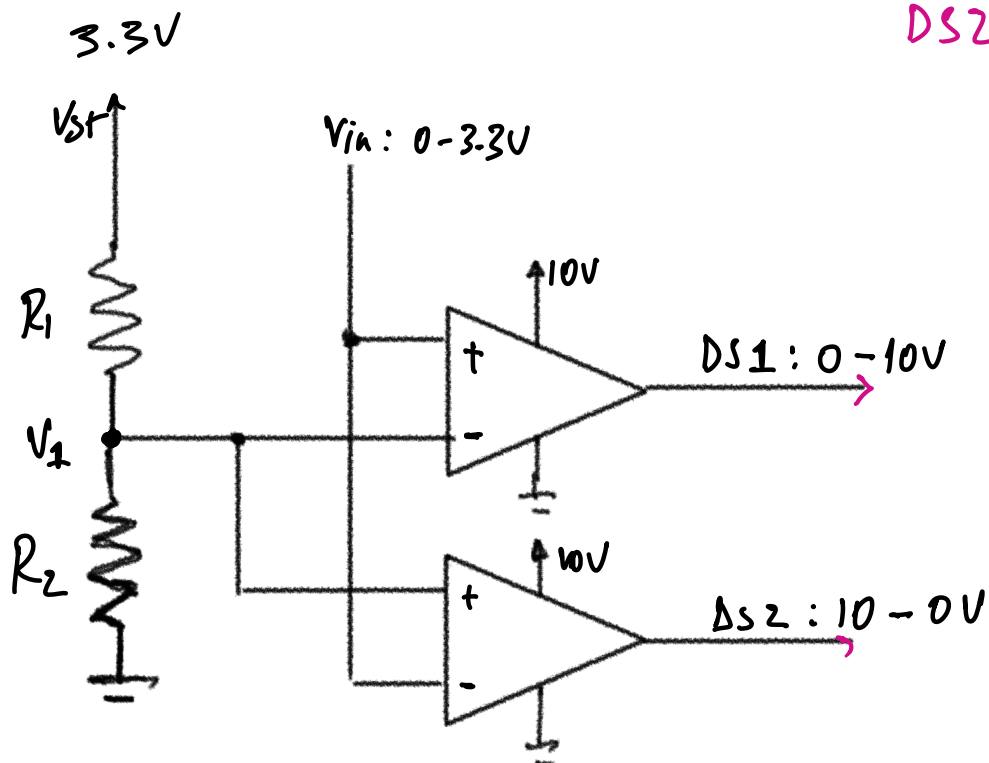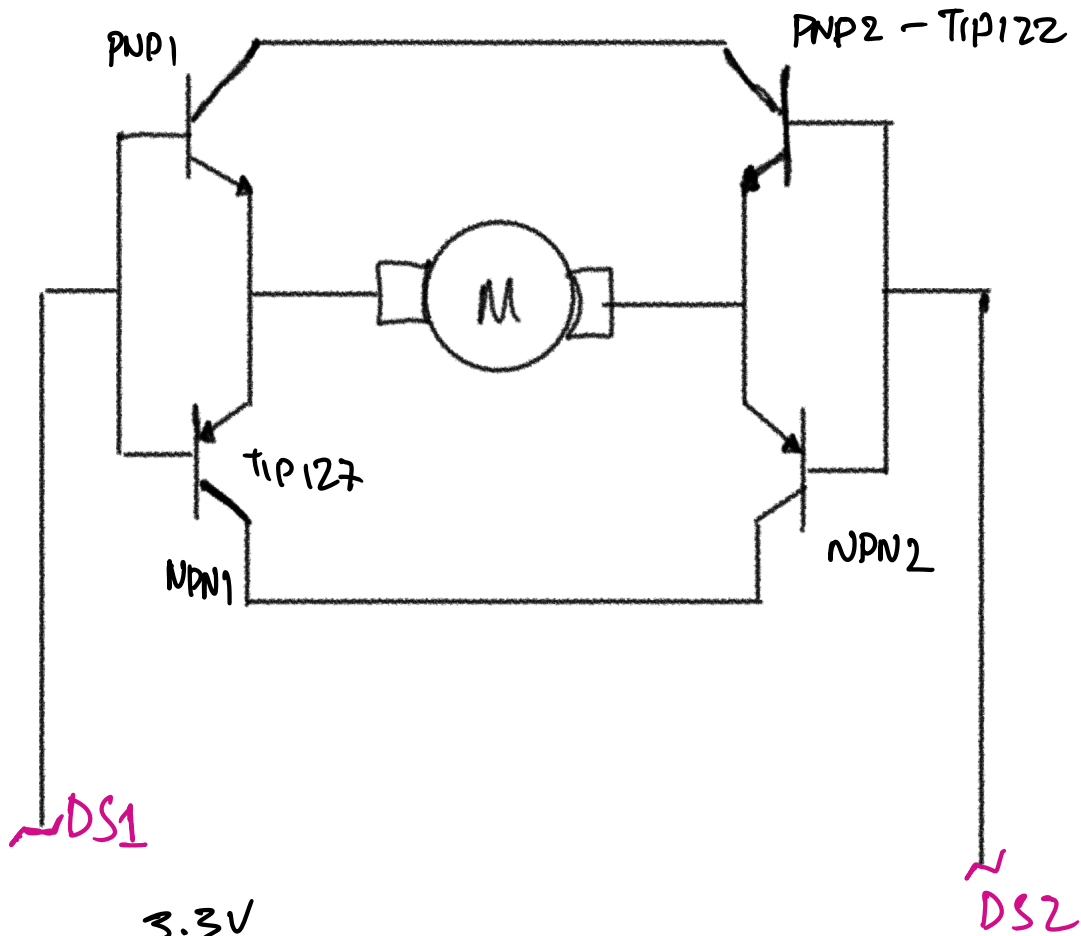

set $V_1 = 1.65V$

Question 1 (6 marks)

$$V_{in} = 0V$$

$$V_+ < V_- : DS1 = 0V$$

$$V_+ > V_- : DS2 = 10V$$

$$V_{in} = 3.3V$$

$$V_+ > V_- : DS1 = 10V$$

$$V_+ < V_- : DS2 = 0V$$

$$i_1 = i_2 \Rightarrow R = \frac{V}{I} \text{ (ohm's) - series}$$

$$\frac{V_{st} - V_1}{R_1} = \frac{V_1 - GND}{R_2}$$

$$\therefore \frac{V_{st} - V_1}{V_1} = \frac{R_1}{R_2}$$

$$\therefore \frac{R_1}{R_2} = 1 \Rightarrow \text{Choose } R_2 = 1.5k\Omega$$

$$\therefore R_1 = R_2 = 1.5k\Omega$$

Question 2 (3 marks)

Output Voltages	$V_{in} = 3.3V$ ($V_{in} > V_{ref}$)	$V_{in} = 0V$ ($V_{in} < V_{ref}$)
V_{out1}	+10V (High)	0V
V_{out2}	0V (Low)	10V

Question 3 (3 marks)

DS1	DS2	PNP1	PNP2	NPN1	NPN2	V across motor
10V	0V	On	off	off	On	$10 - 1.4 = 8.6V$
0V	10V	off	On	On	off	$-(10 - 1.4) =$

Question 4 (14 marks)

Question 5 (6 marks)

K_p increases the rise time & reduces steady-state error magnitude but when too high increases overshoot and potential oscillation.

K_i eliminates the residual steady state error, error elimination faster with higher K_i value. Although it can cause overshoot and slow settling. Excessive integral action results in oscillations.

extra page ...

Question 6 (10 marks)

Question 5

• Sampling time

- * a smaller sampling time will result in more accurate discrete approximation, higher control bandwidth but at the cost of CPU load and noise sensitivity
- * A larger sampling time means CPU overhead will be reduced, but response will be slower, some data could be missed (aliasing) and degraded stability margins.

